



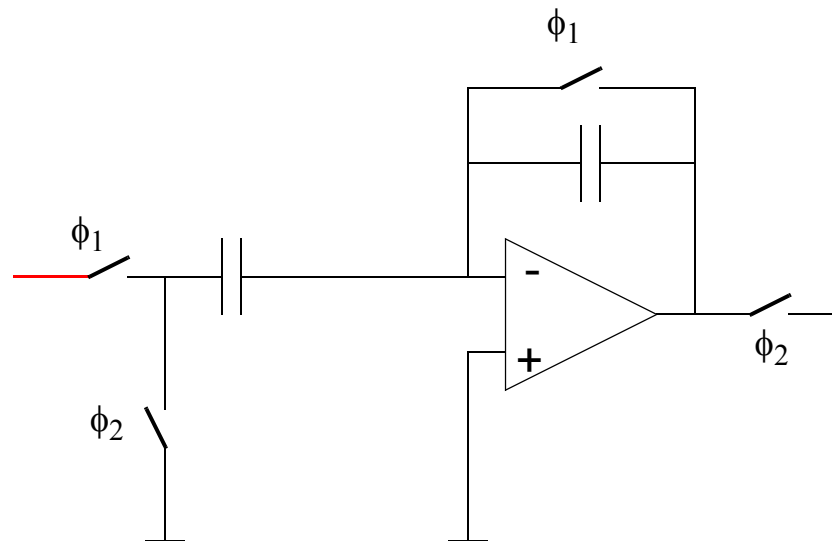
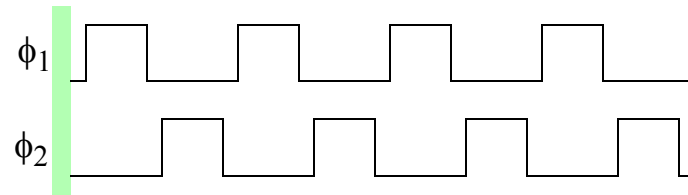
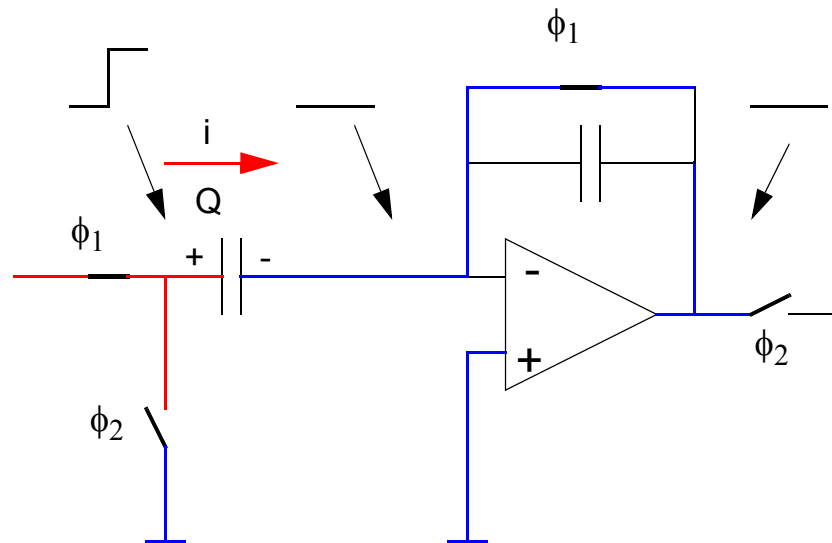
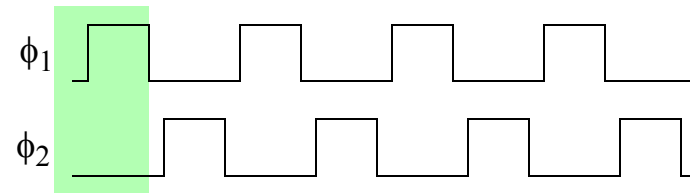




SWITCHED CAPACITOR AMPLIFIERS


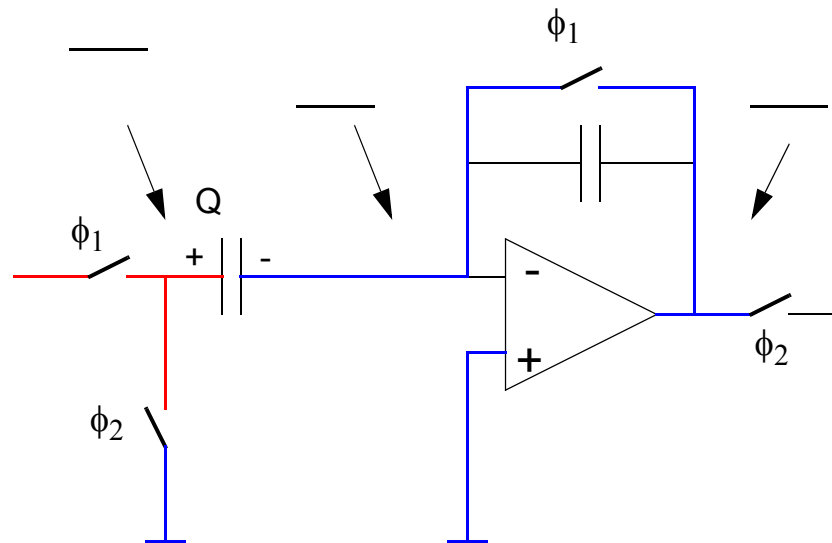



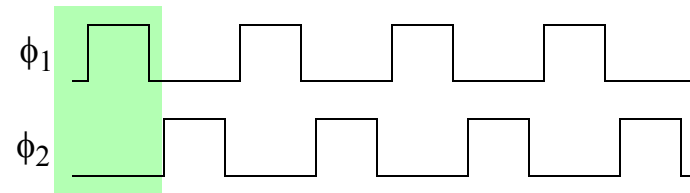



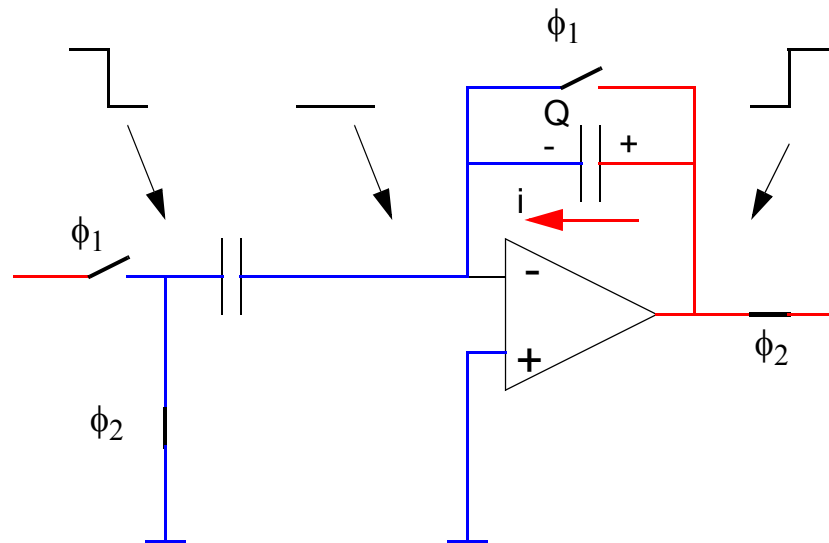


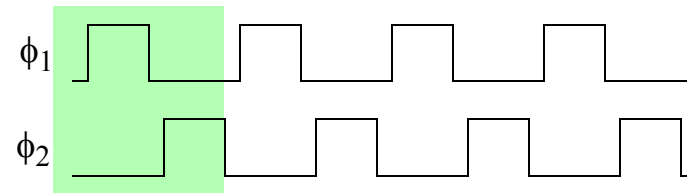

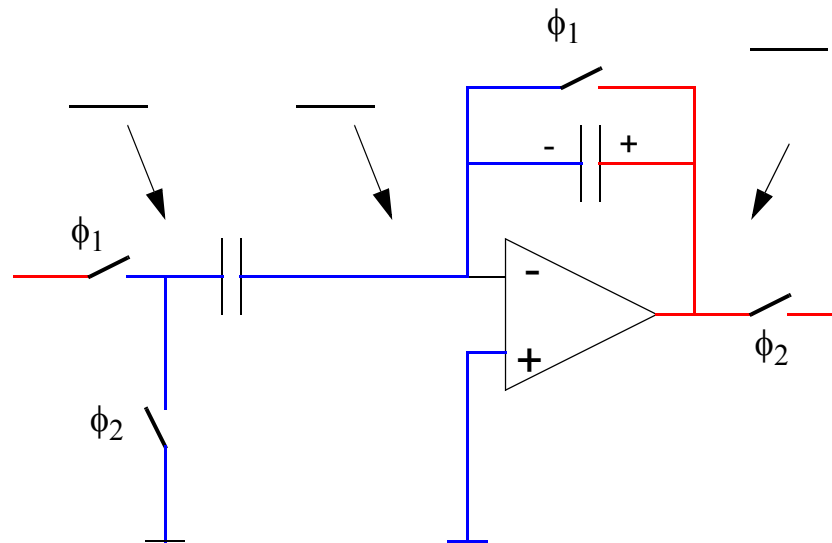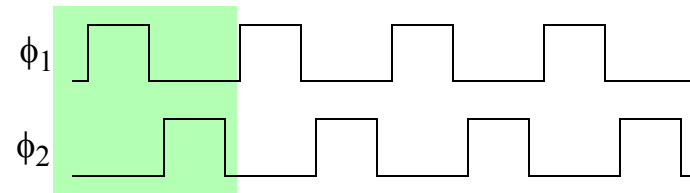

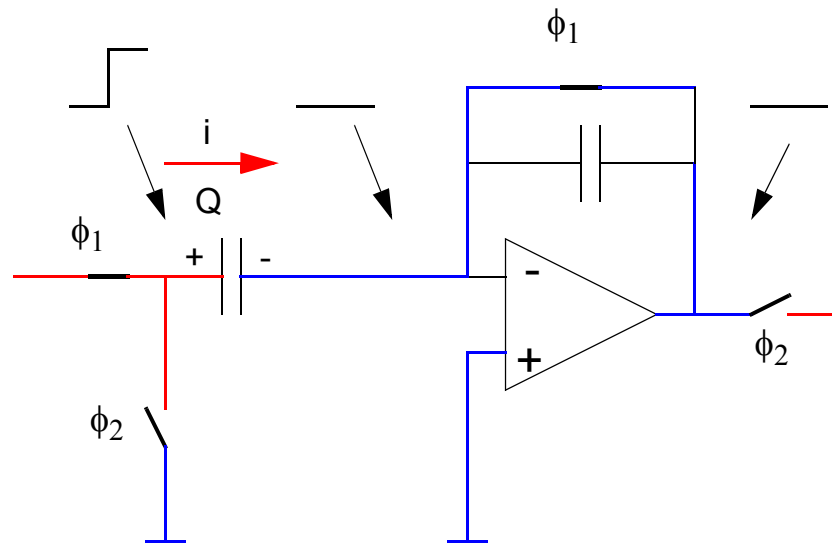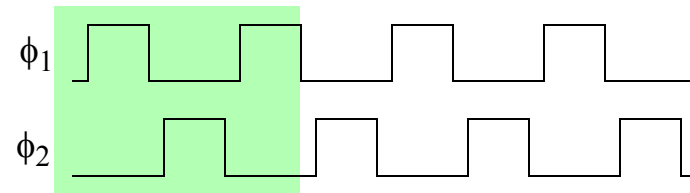

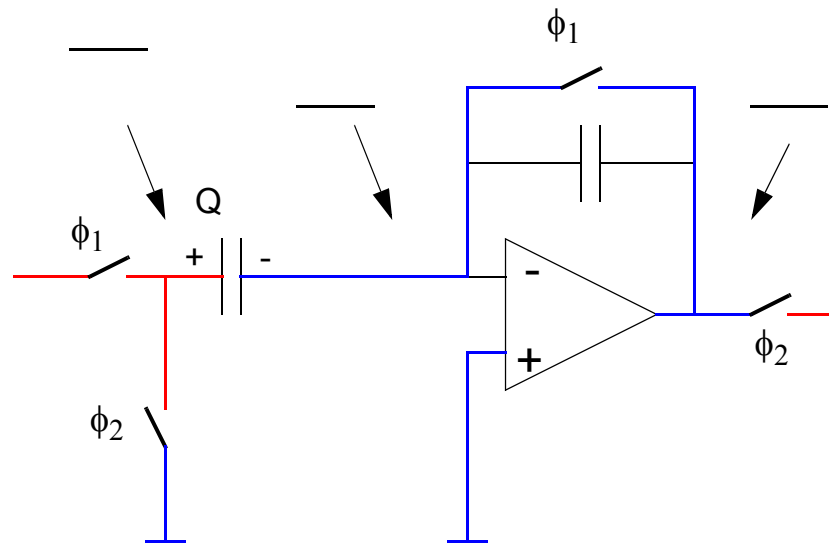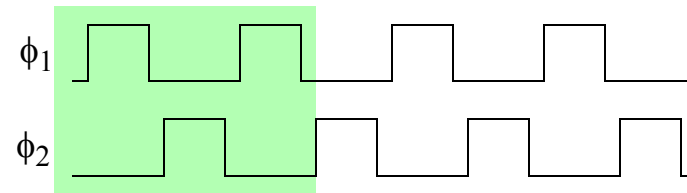

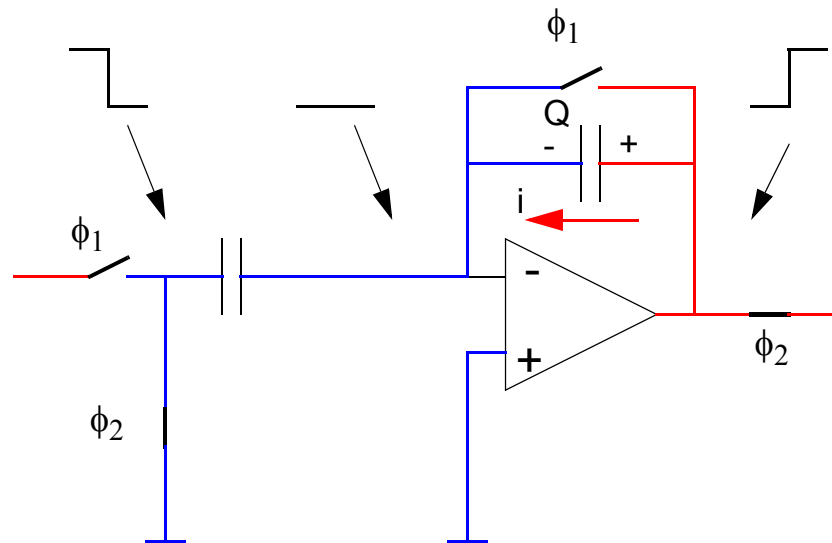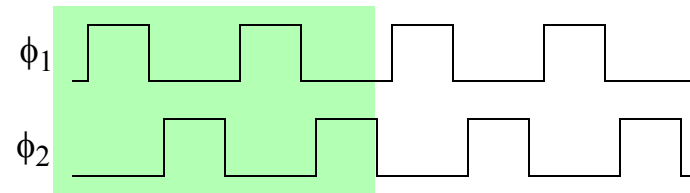

Simple amplifier

First approach: $A_0 = \text{infinite}$.

$$\phi_1: \quad V_{C_1} = V_s - V_x \quad V_{C_F} = 0 \quad V_{\text{out}} = V_x$$

ϕ_2 :

$$V_{C_1} = V_s + \Delta V_s - V_x = -V_x \quad \text{because} \quad \Delta V_s = -V_s$$

$$V_{C_F} = -\frac{\Delta Q_1}{C_F} = -\frac{[-V_x - (V_s - V_x)]C_1}{C_F} = \frac{V_s C_1}{C_F}$$

$$V_{\text{out}} = V_x + V_{C_F} = V_s \frac{C_1}{C_F} + V_x$$

Alternatively:




$$\phi_1: \quad V_{C_1} = -V_x \quad V_{C_F} = 0 \quad V_{\text{out}} = V_x$$

ϕ_2 :

$$V_{C_1} = V_s - V_x$$


$$V_{C_F} = -\frac{\Delta Q_1}{C_F} = -\frac{[V_s - V_x - (-V_x)]C_1}{C_F}$$
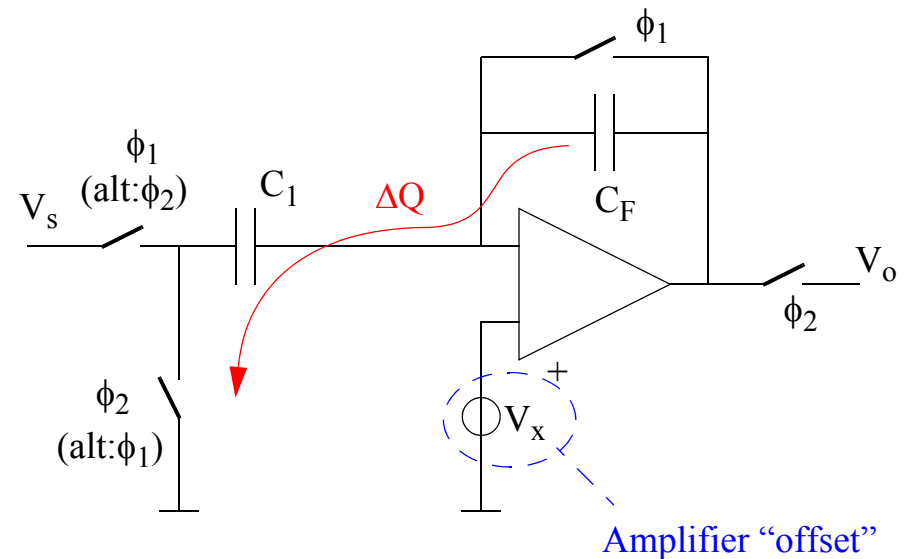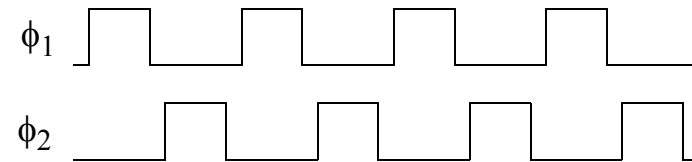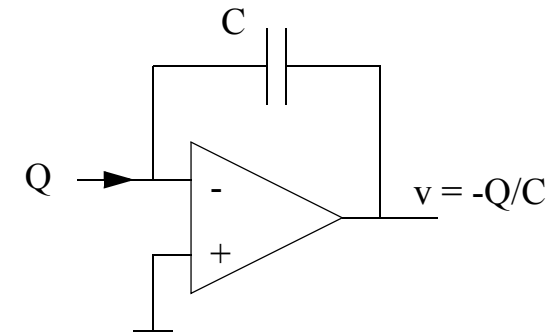
$$V_{\text{out}} = -V_s \frac{C_1}{C_F} + V_x$$




Summing amplifier (ideal):
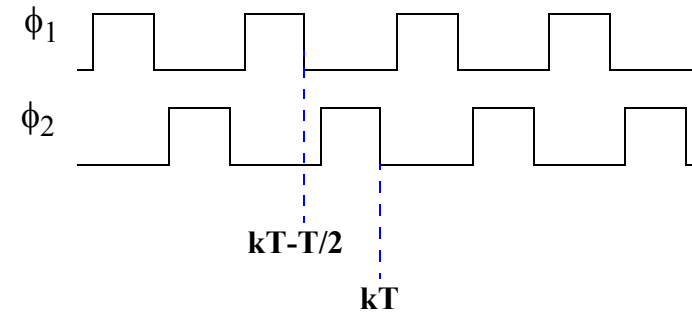
$$V_{\text{out}} = [V_1^p(\phi_1) - V_1^n(\phi_2)] \frac{C_1}{C_F} + [V_2^p\phi_1 - V_2^n\phi_2] \frac{C_2}{C_F} + V_x$$



Generally:
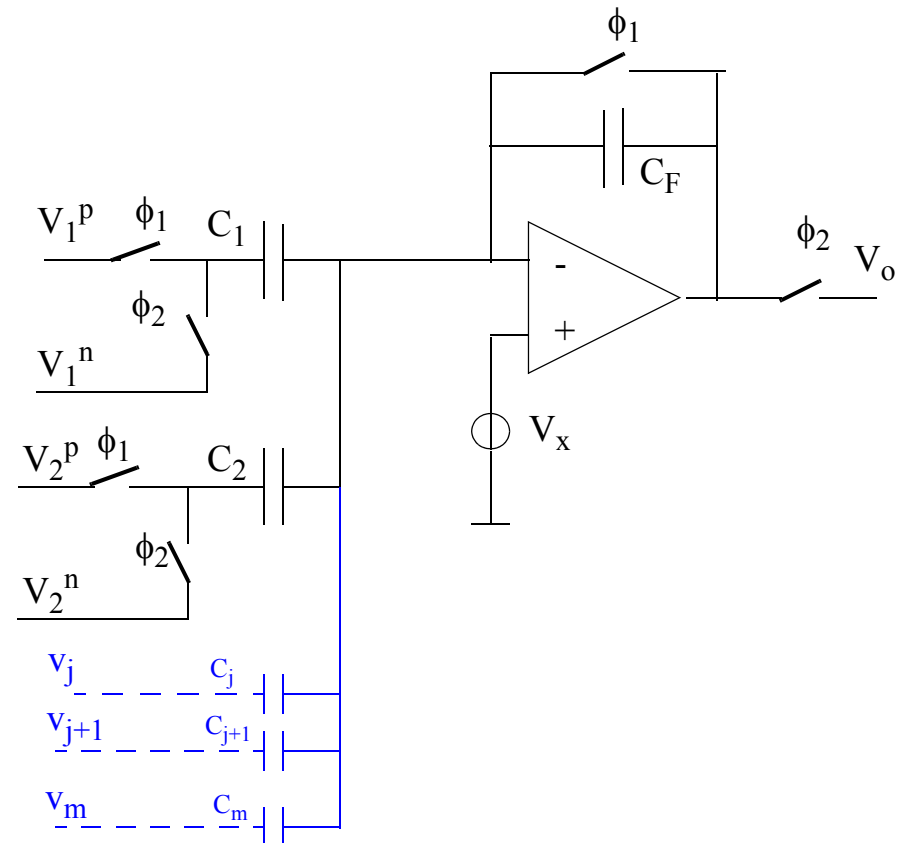
$$V_{\text{out}}(kT) = V_x + \sum_{j=1}^m \frac{C_j}{C_F} [V_j^p(kT - \frac{T}{2}) - V_j^n(kT)] \quad (4.1)$$




Effect of Parasitics

- Final amplifier open loop gain (DC)
- Input offset
- Leak current from sampling capacitors.
- Parasitic capacitance (conductors)

The result is found by applying the super position method on the output signal.

That is the sum of all effects.

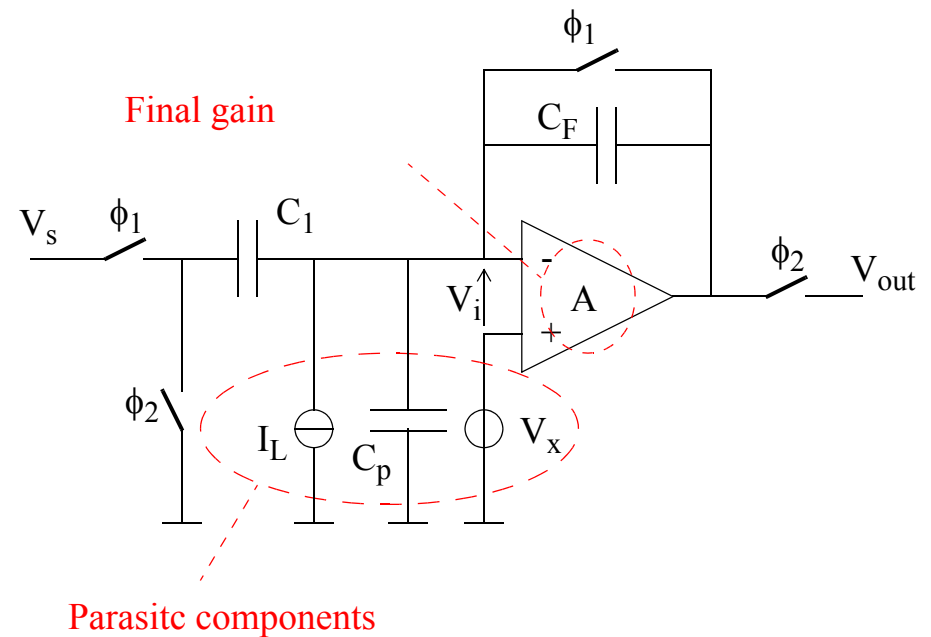


Output signal as a consequence of offset and final gain.

Open loop gain: A

$$V_{\text{out0}} = (V_x - V_{\text{out0}})A$$

$$(A + 1)V_{\text{out0}} = V_x A$$
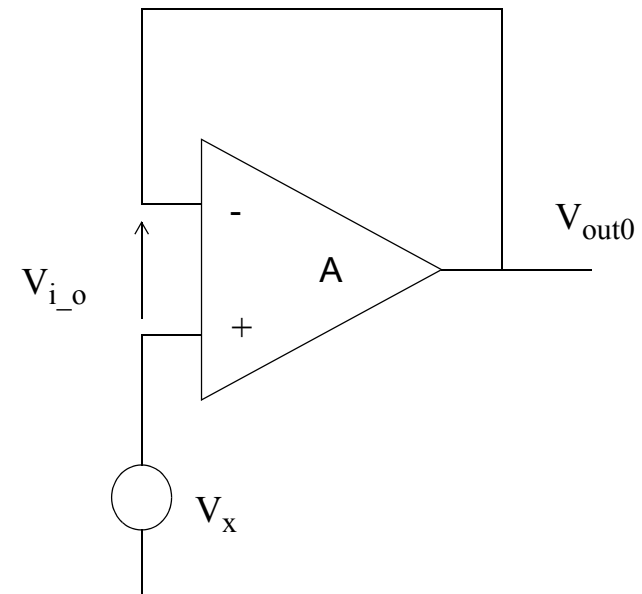
$$V_{\text{out0}} = \frac{A}{1 + A} V_x = \varepsilon_0 V_x \quad (4.2)$$



Output signal as a consequence of final gain and parasitic capacitance.

$$V_{\text{out}} = -V_i A \quad \Delta V_s = -v_s$$

ϕ_1 :

$$V_{C_1} = V_s - V_i = V_s - V_x \frac{A}{1+A} \quad V_{C_F} = 0 \quad V_{\text{out}} = V_x \frac{A}{1+A}$$

ϕ_2 (incremental voltage changes):


$$v_i = -v_s \frac{C_1}{C_1 + C_p + C_F} + v_{\text{out}} \frac{C_F}{C_1 + C_p + C_F}$$

$$v_{\text{out}} = -v_i A = v_s A \frac{C_1}{C_1 + C_p + C_F} - v_{\text{out}} A \frac{C_F}{C_1 + C_p + C_F}$$

$$v_{\text{out}} \left[1 + A \frac{C_F}{C_1 + C_p + C_F} \right] = A v_s \frac{C_1}{C_1 + C_p + C_F}$$

$$v_{\text{out}} = \frac{A v_s \frac{C_1}{C_1 + C_p + C_F}}{1 + A \frac{C_F}{C_1 + C_p + C_F}} = \frac{A v_s C_1}{C_1 + C_p + C_F + A C_F}$$

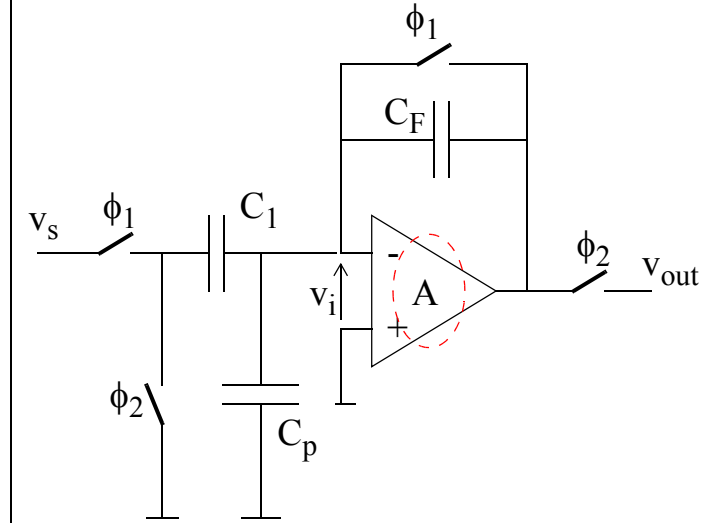
$$v_{\text{out}} = \frac{C_1}{C_F} \frac{A}{1 + (C_1 + C_p)/C_F + A} v_s = \frac{C_1}{C_F} \frac{1}{1 + \varepsilon_A^1} v_s$$



$$\varepsilon_A^1 = \frac{1}{A} \frac{(C_p + C_F + C_1)}{C_F} \quad (4.3)$$

Output signal as a consequence of leak current I_L in the pulse period τ .
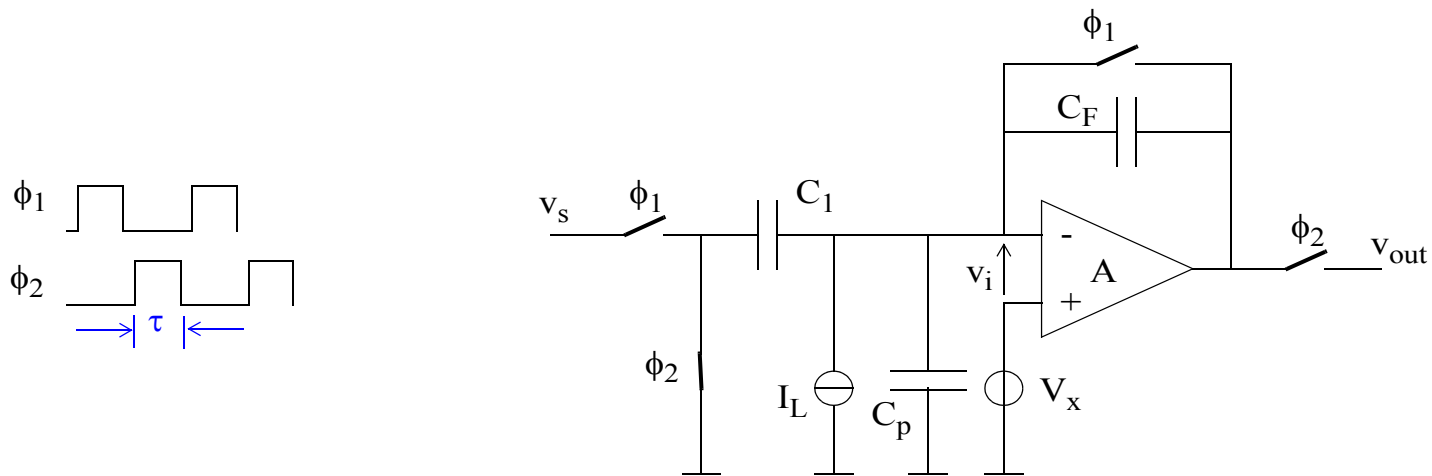
$$v_{\text{outL}} = \frac{C_1 + C_p}{C_F} \frac{1}{1 + \varepsilon_A} \frac{I_L \tau}{C_1 + C_p} = \frac{I_L \tau}{C_F(1 + \varepsilon_A)} = \frac{I_L \tau A}{C_1 + C_p + C_F(1 + A)} \quad (4.4)$$



Final result

Summing (4.2), (4.3) and (4.4):

$$v_{\text{out}} = \frac{C_1}{C_F} \frac{1}{1 + \varepsilon_A} v_s + \frac{I_L \tau}{C_F(1 + \varepsilon_A)} + \frac{A V_x}{1 + A} \quad (4.5)$$

Offset Compensation

ϕ_1 : V_x is sampled, C_F is charged to V_x

ϕ_2 : When $Q = \Delta V_s C_1$ is transferred to C_F , V_x is already across C_F with the negative charge at the amplifier output (when V_x is positive)

ϕ_1 :


$$V_{C_1} = V_s - V_x \quad V_{C_F} = V_x \quad V_{out} = V_x$$

ϕ_2 :

$$V_{C_1} = (V_s - V_x) + \Delta V_s = -V_x$$


$$\Delta V_{C_F} = -\frac{\Delta Q_1}{C_F} - V_x = -\frac{[-V_x - (V_s - V_x)]C_1}{C_F} - V_x$$
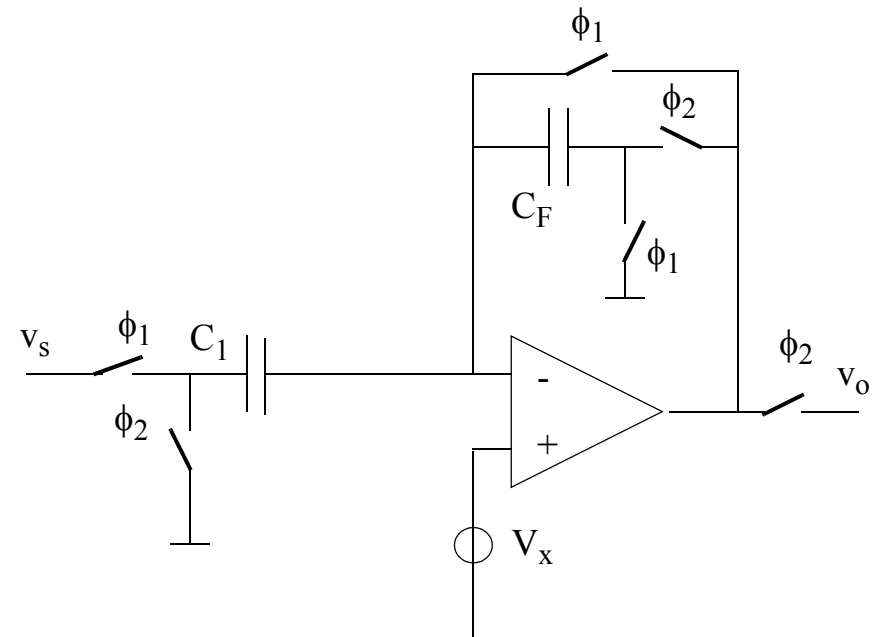
$$V_{out} = V_x + V_s \frac{C_1}{C_F} - V_x = V_s \frac{C_1}{C_F}$$




Compensation of charge injection:

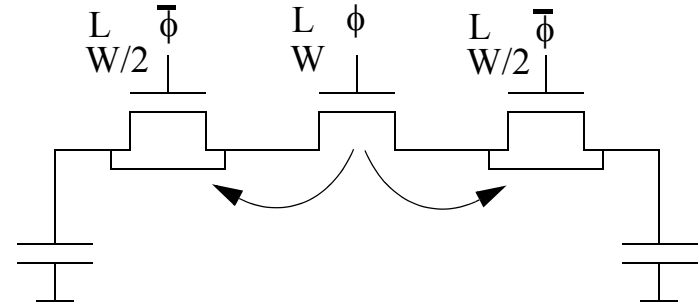Add dummy switches that are clocked in anti phase with the real switches.



Compensation of charge injection and clock feed through:

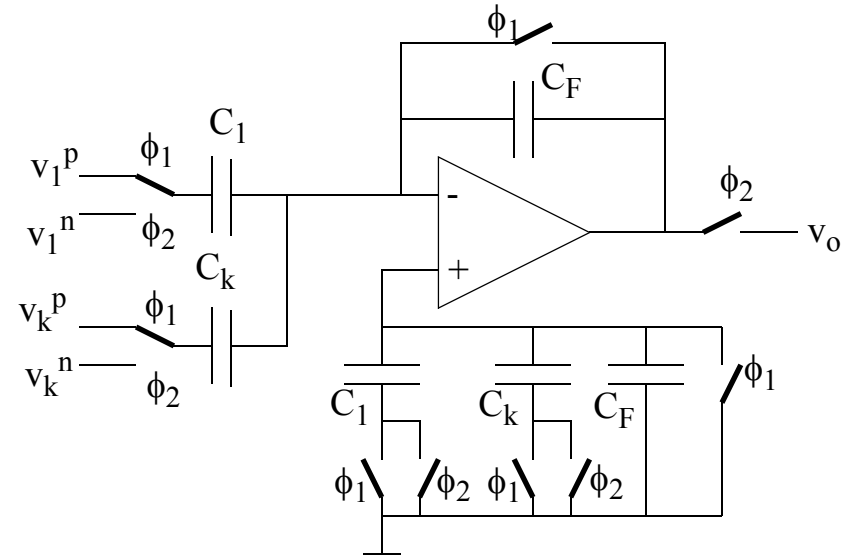Introduce corresponding switches and capacitance on both amplifier's input terminals.







Dynamical Properties of SC Amplifiers

g_m : Amplifier transconductance, determined by the transconductance of the input transistors.

r_o : Amplifier output resistance

C_L : Load capacitance of the configuration.

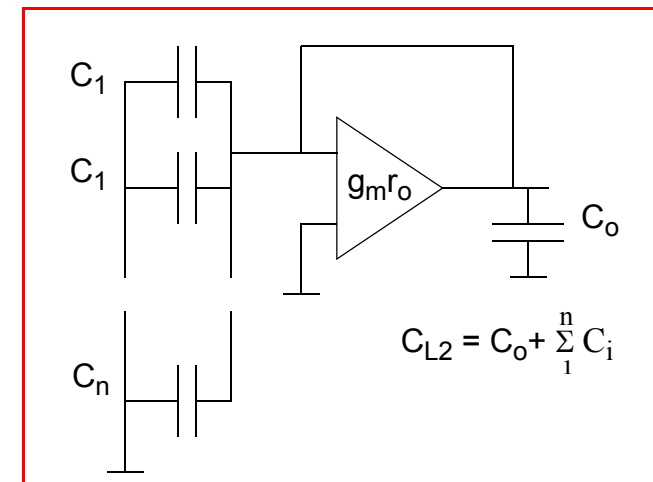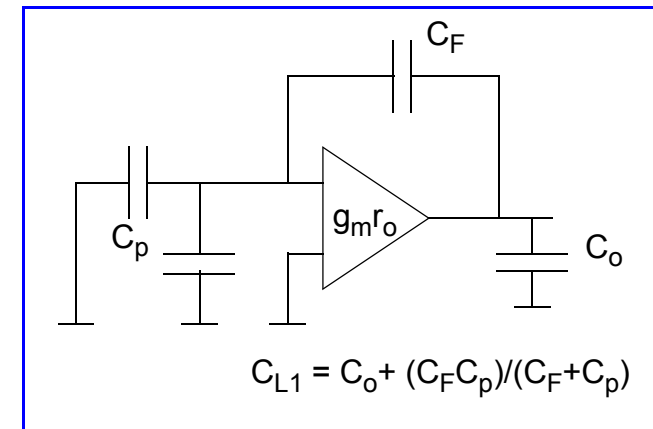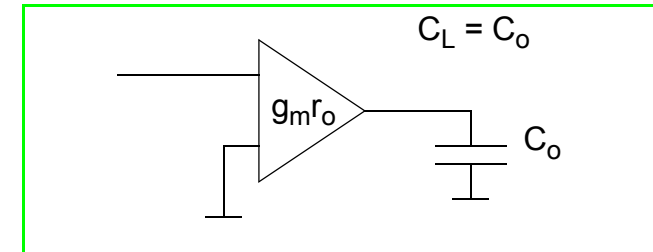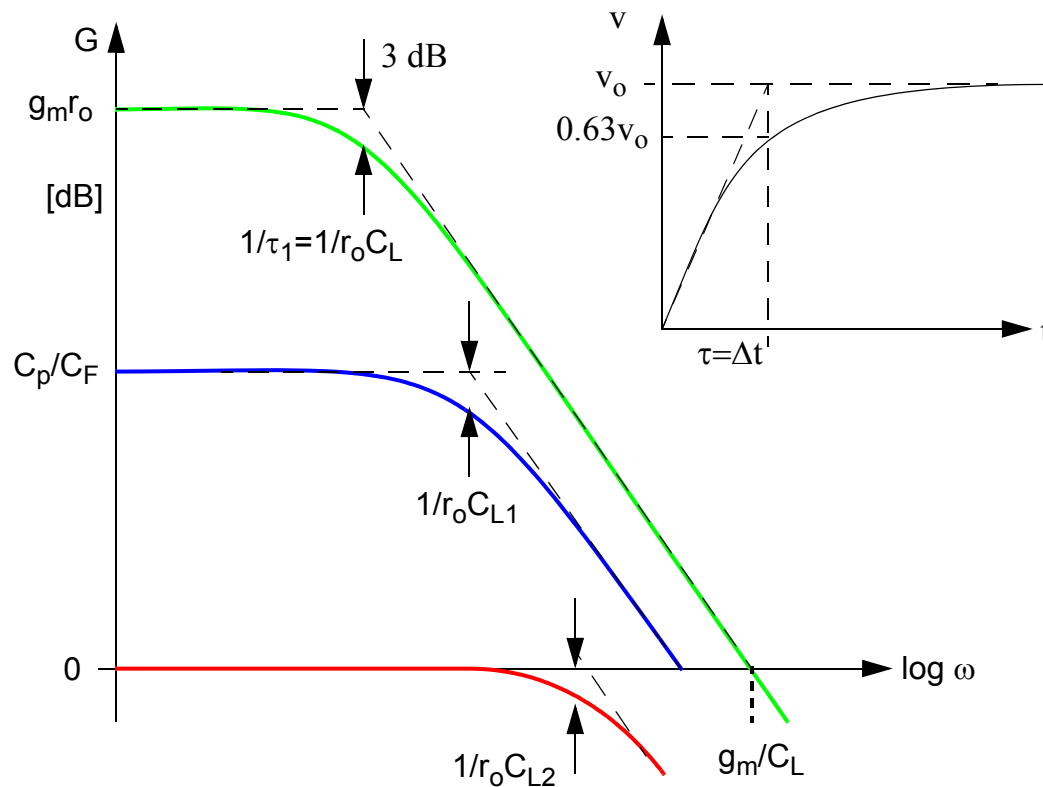C_p : Parallel capacitance of the input node



Requirements on the time constant:

$$v_o = v_{o,ss}(1 - e^{-t/\tau})$$


$$\left. \frac{dv_o}{dt} \right|_{t=0} = v_{o,ss} \frac{1}{\tau} e^{-t/\tau} \Big|_{t=0} = \frac{v_{o,ss}}{\tau}$$

Settling to 1% of $v_{o,ss}$ set the following requirement to t_s :

$$e^{-t_s/\tau} = 0,01$$



$$t_s = (-\tau) \ln 0,01 = 4,6\tau$$

$$\tau = \frac{t_s}{4,6}$$

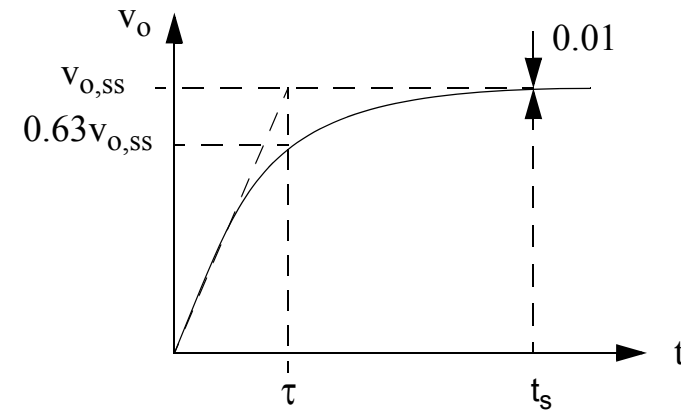

Instrumental Amplifiers

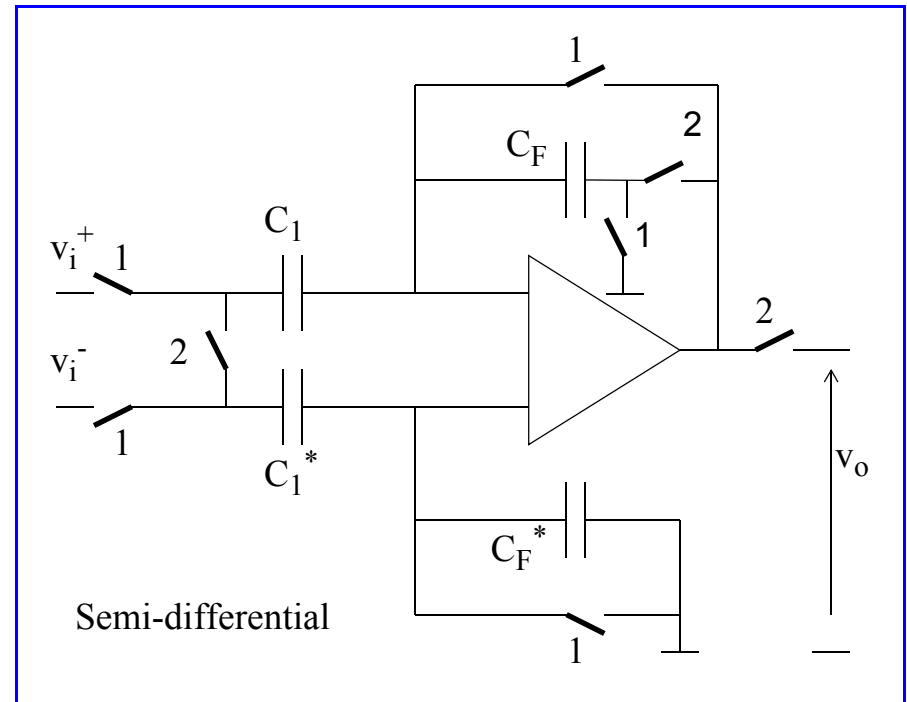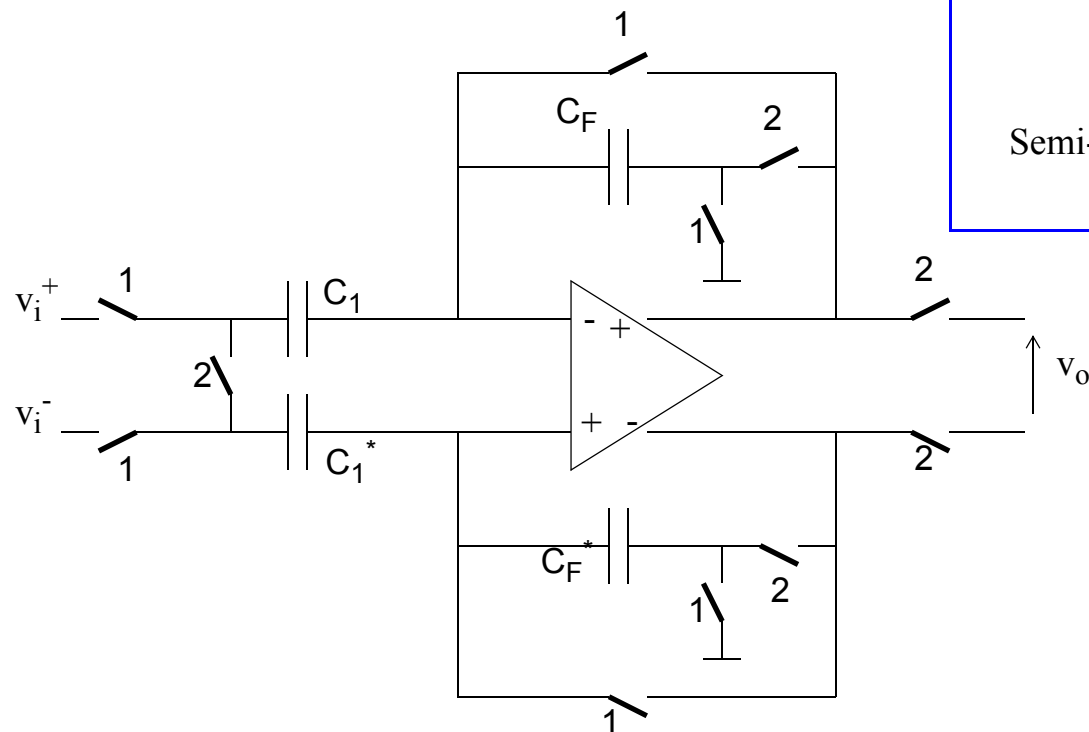
- Correlated double sampling
Phase 1: Offset and LF noise are stored at the input
Phase 2: Subtracted from the amplified signal.
- Differential topology
Reduces charge injection and clock feed through.
Reduces non linearity in capacitors (distortion)
Improves PSSR (Power Supply Rejection Ratio)




$$v_o = (v_i^+ - v_i^-) C_1 / C_F$$

READ-OUT CHAIN ARCHITECTURE


Column read out (principle)

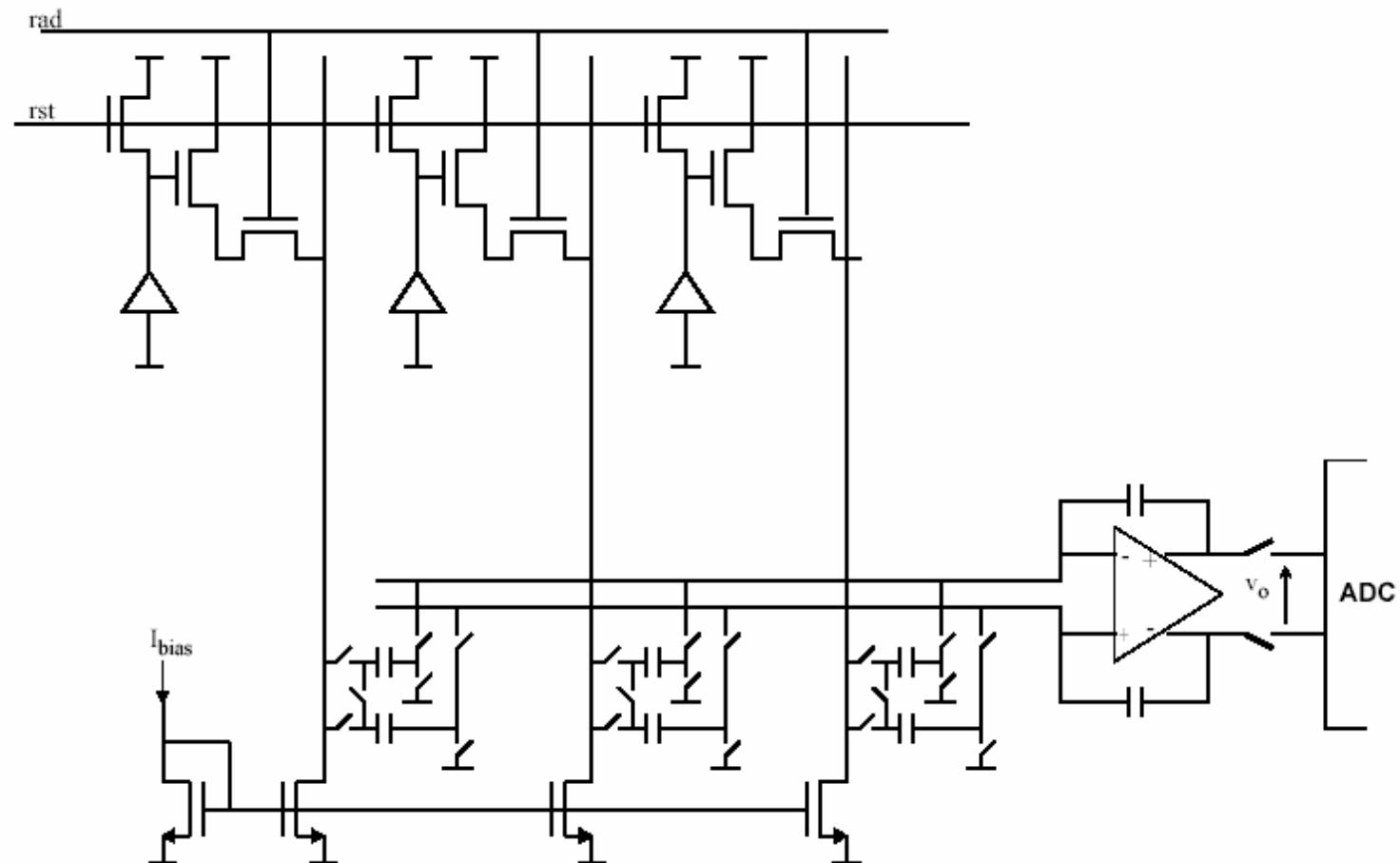

Column read out (cont.)

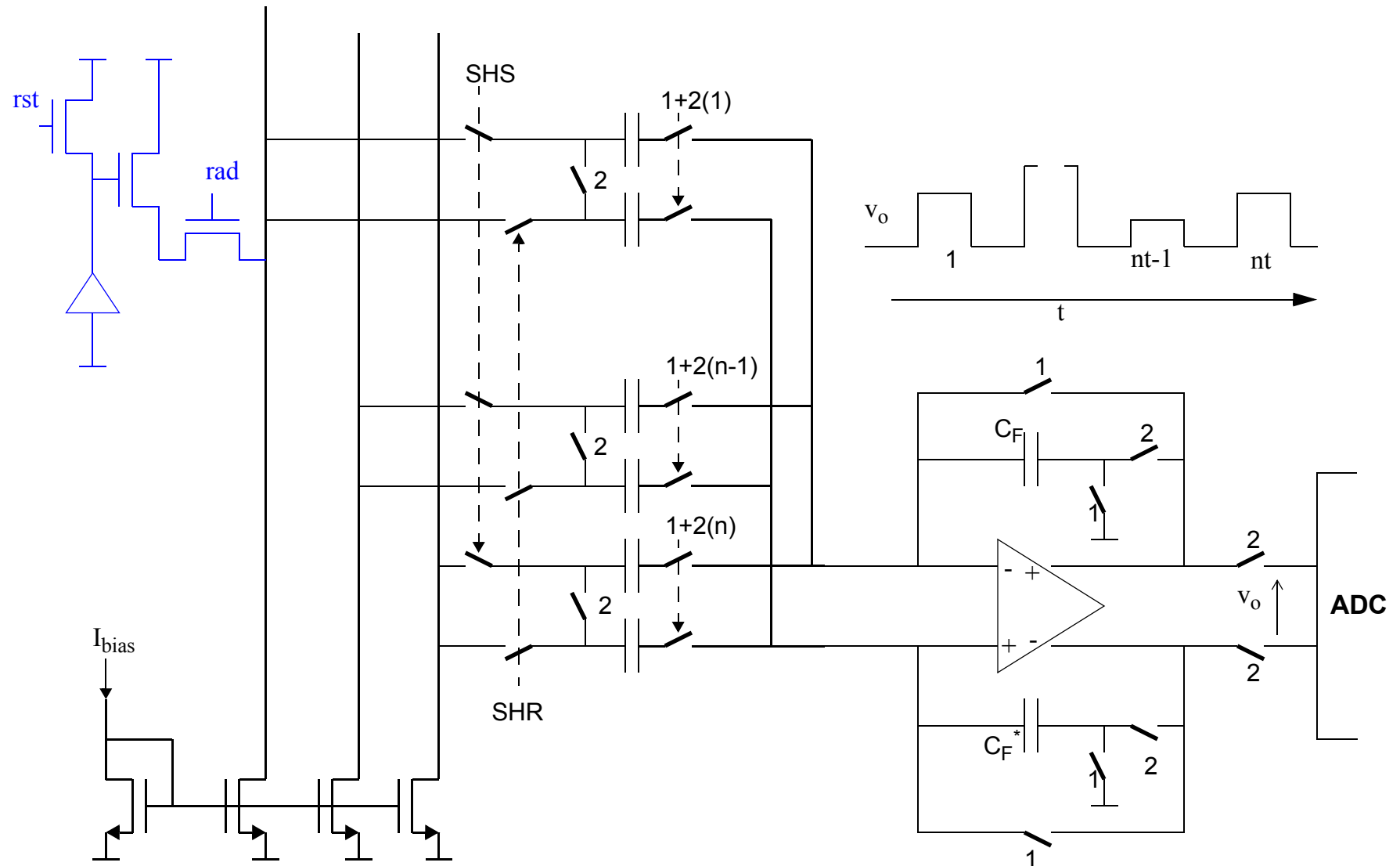

Read out time diagram

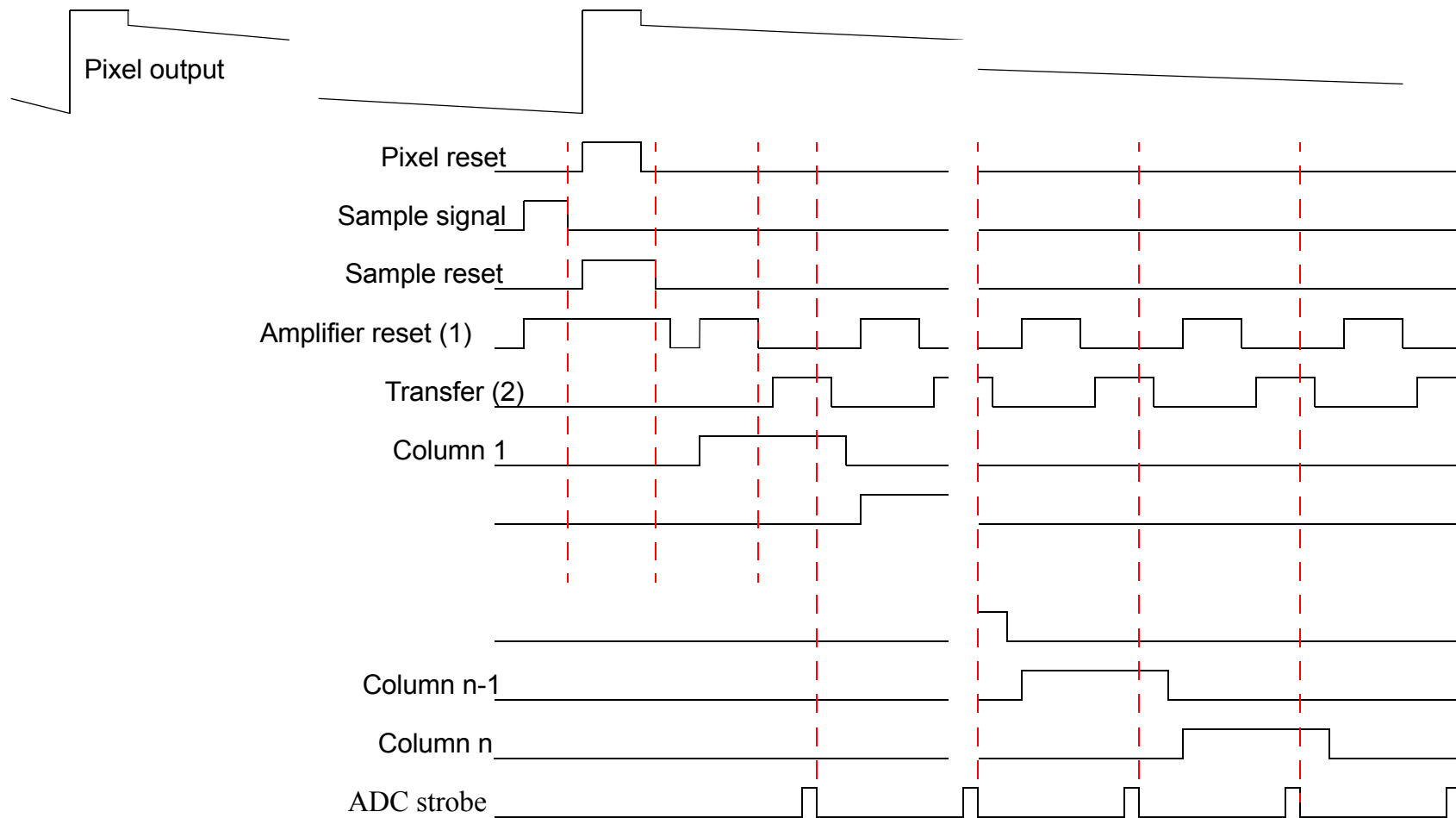


**Column parallel
read out
(example)**

Slow ADC is OK:


Successive
ApproximationSingle slope
(common to all columns)

Cyclic

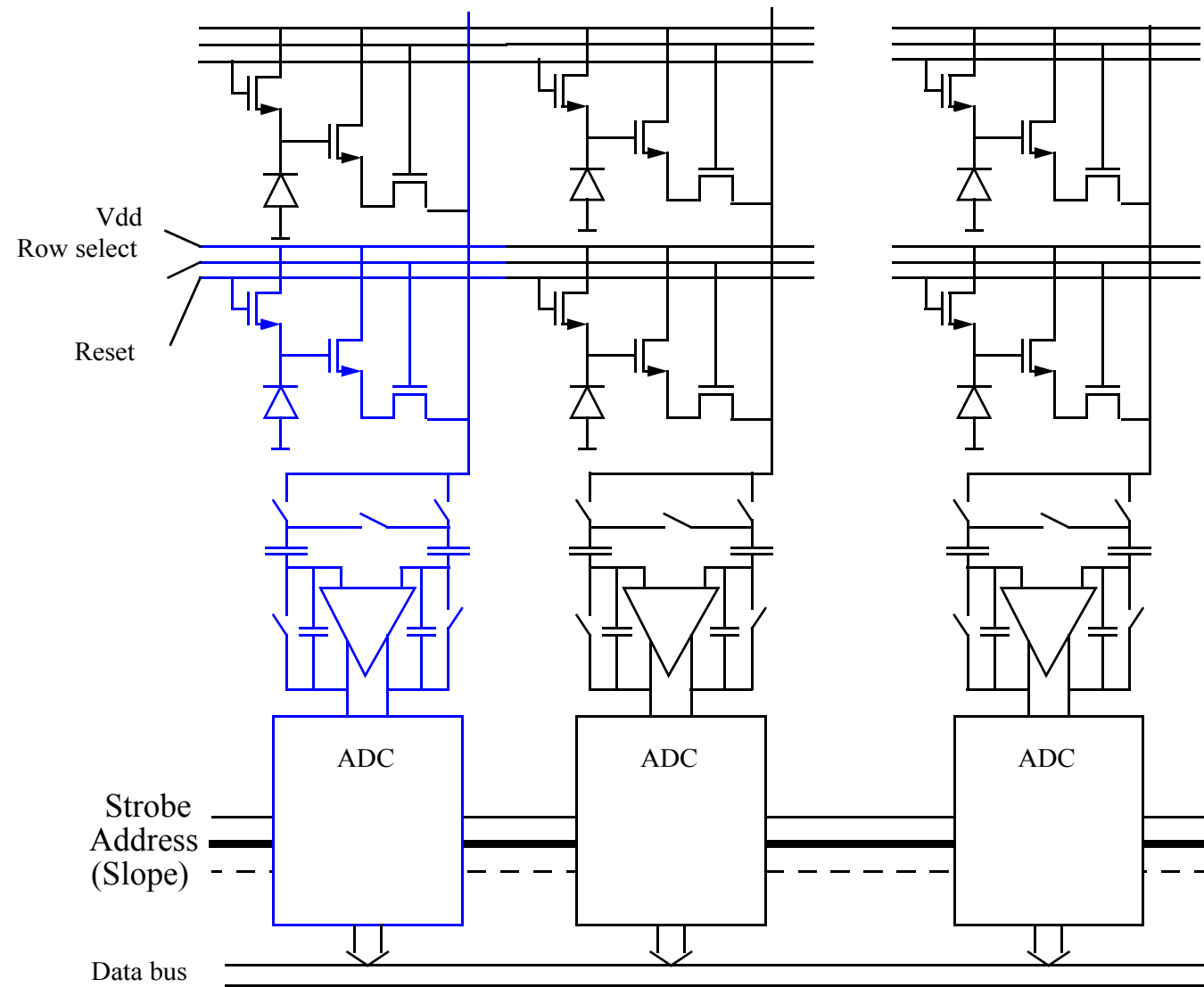


Synchronizing

Mechanical shutter
Synchronized with
ERS

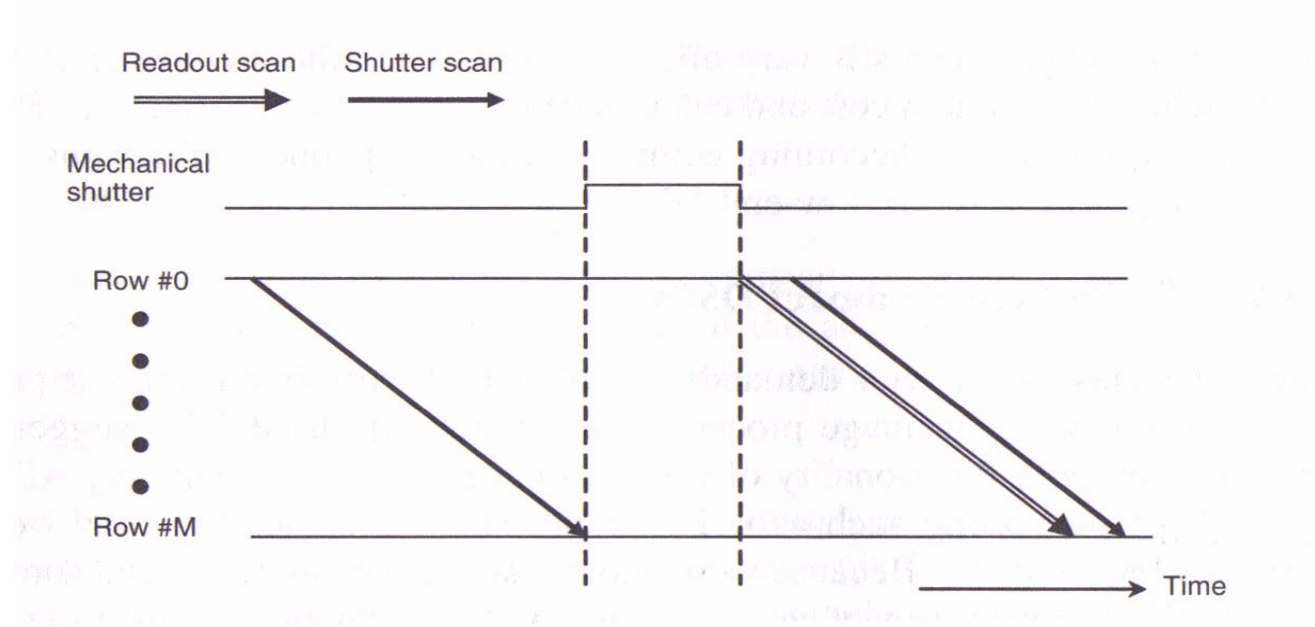


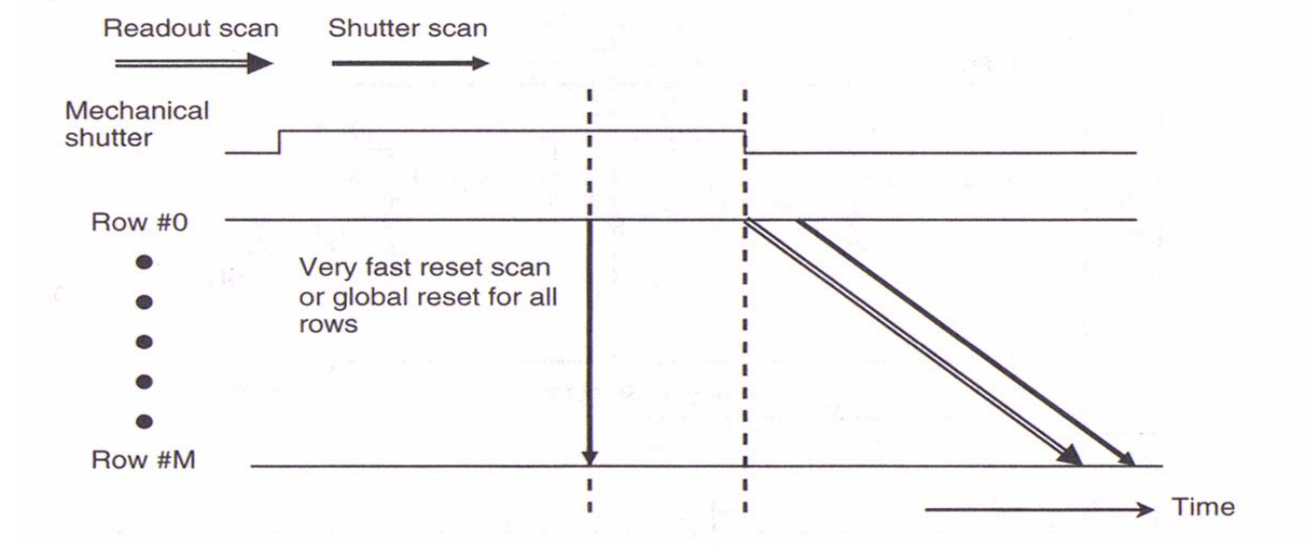Mechanical shutter
Synchronized with
Global Reset



Synchronizing (cont.)


Electronic global shutter

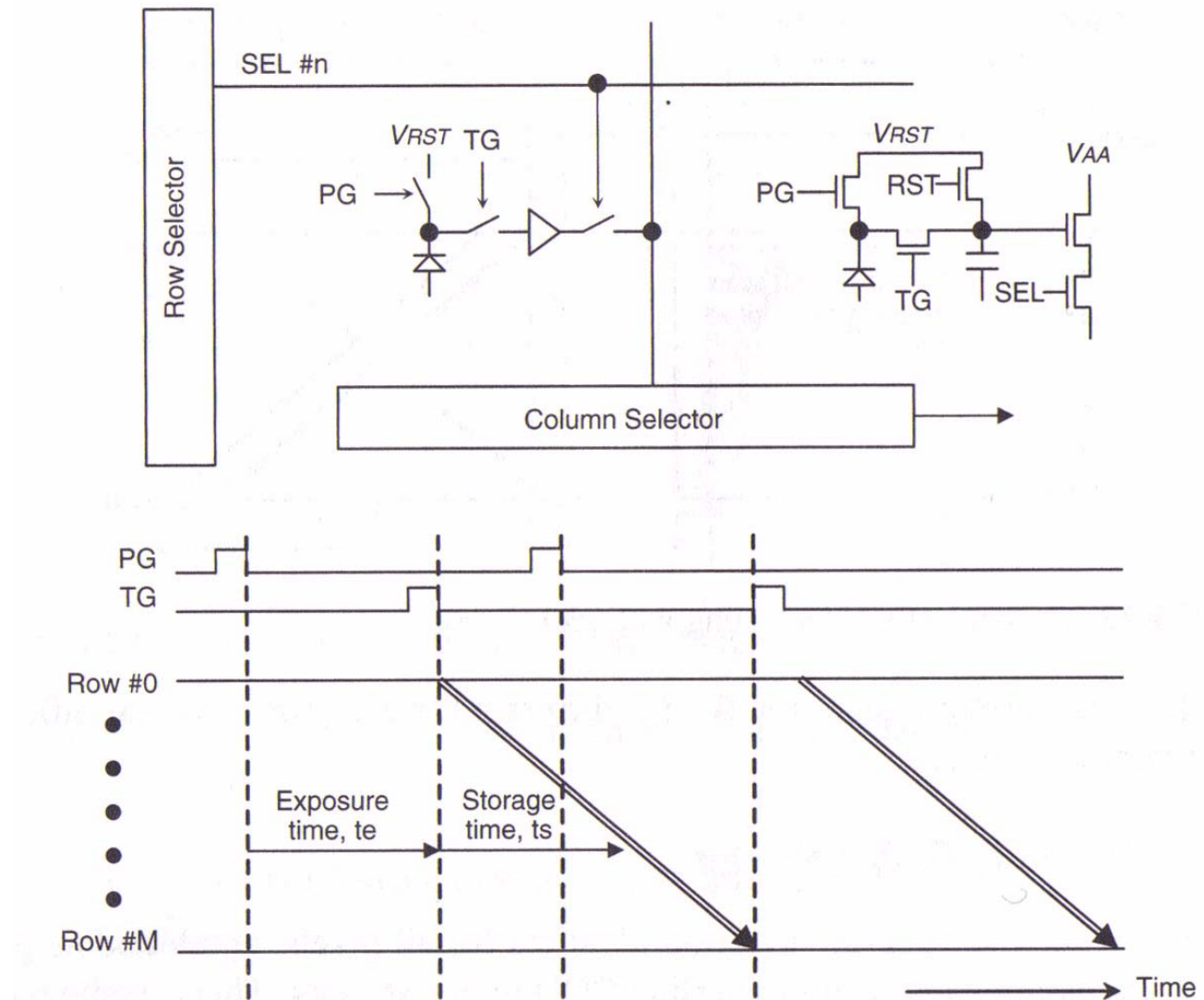


Reduced resolution but higher frame rates

Skipping

- + Simple solution
- Aliasing

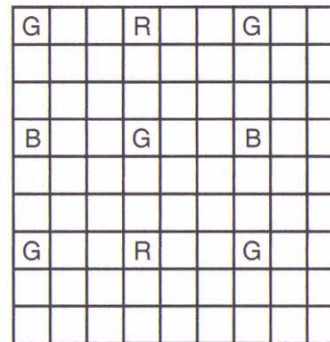


(a) Constant pitch skipping

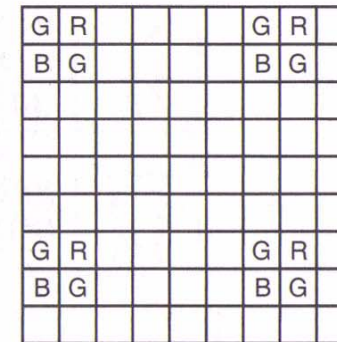

(b) Pseudo-pixel pitch skipping

Binning

- + Spatial LP filter
- More complex

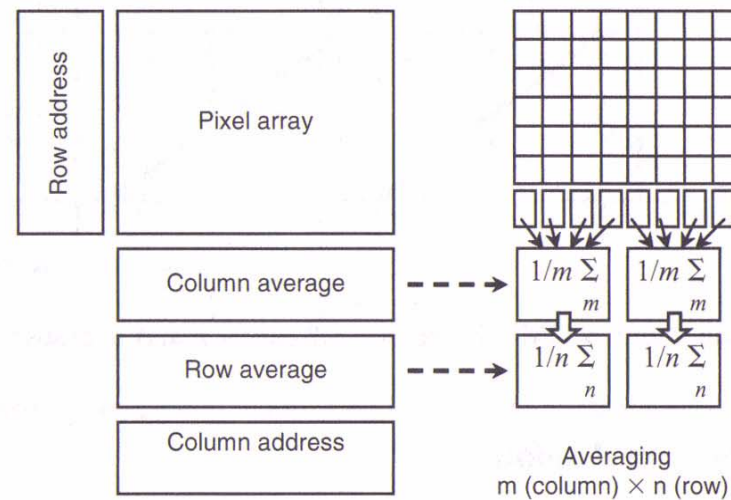

References:

Unbehauen:

MOS Switched-Capacitor and Continuous-Time Integrated Circuits and Systems
Rolf Unbehauen, Andrzej Cickocki
Springer-Verlag

Nakamura:

Image Sensors and Signal Processing for Digital Still Cameras,
edited by Junich Nakamura
Taylor & Francis